

## Practical Part C: CMOS Implementation




To prepare CMOS layout in selected technology, simulate with and without capacitive load, comment on rise, and fall times.

**Practical :** Design and implementation of Layout using CMOS 0.25 micron Technology in Microwind.

 - A. Inverter
- B. NAND
- C. NOR

PMOS completed

now interconnection of PMOS and NMOS to complete inverter  
connect source of PMOS to VDD and source of NMOS to VSS  
short the drain of both PMOS and NMOS



## Practical

### Part C: CMOS Implementation




To prepare CMOS layout in selected technology, simulate with and without capacitive load, comment on rise, and fall times.

**Practical :** Design and implementation of Layout using CMOS 0.25 micron Technology in Microwind.

A. Inverter

B. **NAND**

C. NOR

 

## Practical Part C: CMOS Implementation


To prepare CMOS layout in selected technology, simulate with and without capacitive load, comment on rise, and fall times.

**Practical :** Design and implementation of NOR Gate Layout using CMOS 0.25 micron Technology in Microwind.

A. Inverter

B. NAND

C. **NOR**

 

## Practical


### Part C: CMOS Implementation of 2:1 Mux using TG



To prepare CMOS layout in selected technology, simulate with and without capacitive load, comment on rise, and fall times.

**Practical:** Design and implementation of 2:1 Mux Layout using CMOS 0.25 micron Technology in Microwind.

Sel	Y
0	B
1	A

 

Inputs			Q
A	I <sub>1</sub>	I <sub>0</sub>	
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# One Bit SRAM Cell

